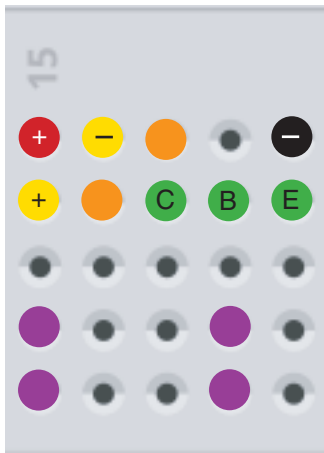




Single transistor touch switch breadboard layout




-  Battery +
-  Battery -
-  LED
-  Resistor
-  Transistor
-  Copper wire

LED pins



BC547 NPN
transistor pins

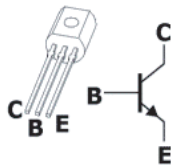

Parts list:

1 NPN transistor

1 220 ohm resistor

1 LED

1 Dual AA battery holder (3 volts)

3" 20 ga. bare copper wire

Project page: <http://hackaweek.com/hacks/?p=1549>